



Samueli
School of Engineering

CS-M151B

Computer Systems Architecture


Blaise
UCLA Computer
Science

Review: Digital Circuits

Combinational Circuits

Combinational circuits

 
- Output depends on current inputs only
- Consist of a connection of multiple logic gates
 - And/Or/Not



Combinational Circuits

Combinational circuits

- Example1

 

```
module SystemX (output wire F,
                input  wire A, B, C);

    wire  An, Bn, Cn;    // internal nets
    wire  m0, m2, m6;

    assign An = ~A;      // Not's
    assign Bn = ~B;
    assign Cn = ~C;

    assign m0 = An & Bn & Cn; // AND's
    assign m2 = An & B  & Cn;
    assign m6 = A  & B  & Cn;


    assign F  = m0 | m2 | m6; // OR

endmodule
```

Combinational Circuits

Combinational circuits

- Example2: multiplexer

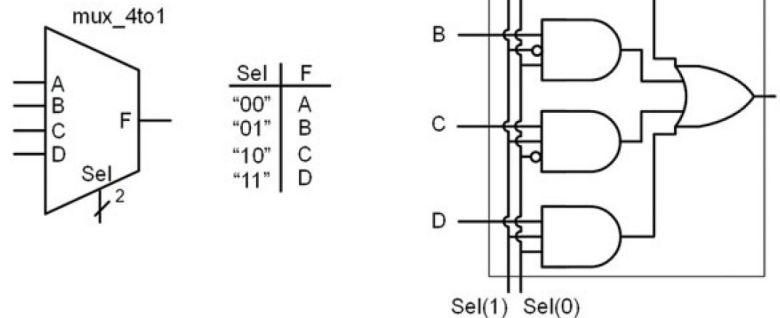


The following shows how to model the behavior of the mux using continuous assignment and logical operators.

```
module mux_4to1 (output wire F,  
    input wire A, B, C, D,  
    input wire [1:0] Sel);  
  
    assign F = (A & ~Sel[1] & ~Sel[0]) |  
        (B & ~Sel[1] & Sel[0]) |  
        (C & Sel[1] & ~Sel[0]) |  
        (D & Sel[1] & Sel[0]);  
  
endmodule
```

Sequential Circuits

Sequential circuits

 - Output depends on current inputs and prior state
- Need a storage/memory to hold prior state
- e.g. storage element
 - D-flip-flops
 - RAMs




Sequential Circuits

D-Flip-flop:

- Digital storage element
- Input is propagated to output at the rising edge of the clock
- **Registers are implemented using D-Flip-flops**

 Example: Behavioral Model of a D-Flip-Flop in Verilog




Clk	D	Q	Qn	
0	X	Last Q	Last Qn	Store
1	X	Last Q	Last Qn	Store
┐	0	0	1	Update
┐	1	1	0	Update

```
module dflipflop (output reg Q, Qn,  
                  input wire Clock, D);  
  
    always @ (posedge Clock)  
    begin  
        Q <= D;  
        Qn <= ~D;  
    end  
  
endmodule
```

Applications of D-Flip-Flop


D-Flip-flop are use for:

 - Data storage
- Data synchronization
- Finite state machines
- Pipelining
- **Timing resolution**
 - Reduced propagation delay of combinational blocks
 - Improve clock speed



Propagation Delay and Critical Path

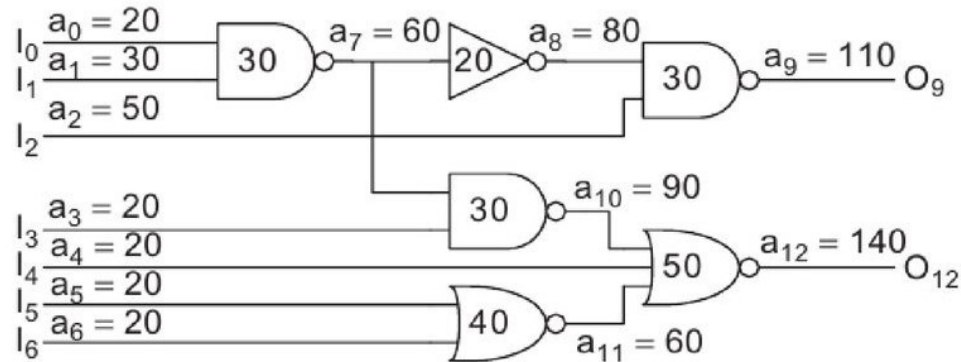- **Propagation delay** (T_p)
 - Time needed for the gate to respond to a change at its inputs
 - $F = 1 / T_p$
- **Critical path** is the longest propagation delay in the circuit between I/O or registers
 - $F_{max} = 1 / T_{max}$




9

Finite State Machines

Definition: State-driven model of computation to design sequential circuits.

Mealy type FSM

 
- (state, input) \rightarrow output
- Pros: Smaller number of FSM states
 - Some input directly contribute to output
- Cons: Input critical path
 - Why?



Finite State Machines

Moore type FSM

 - (state) \in output
- Pros: High-speed
 - Why?
- Cons: Large number of states
 - due to full inputs handling
 - can affect circuit size



RISC-V CPU Implementation

Basic RISC-V CPU Datapath

RISC-V ISA subset:

- R-type
- I-type
- LD/ST
- Branch

0000000	rs2	rs1	000	rd	0110011	ADD
0100000	rs2	rs1	000	rd	0110011	SUB
0000000	rs2	rs1	110	rd	0110011	OR
0000000	rs2	rs1	111	rd	0110011	AND

imm[11:0]	rs1	000	rd	0010011	ADDI
imm[11:0]	rs1	110	rd	0010011	ORI
imm[11:0]	rs1	111	rd	0010011	ANDI


imm[11:0]	rs1	010	rd	0000011	LW
imm[11:5]	rs2	rs1	010	imm[4:0]	SW

imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ
--------------	-----	-----	-----	-------------	---------	-----

Basic RISC-V CPU Datapath

Basic Steps:

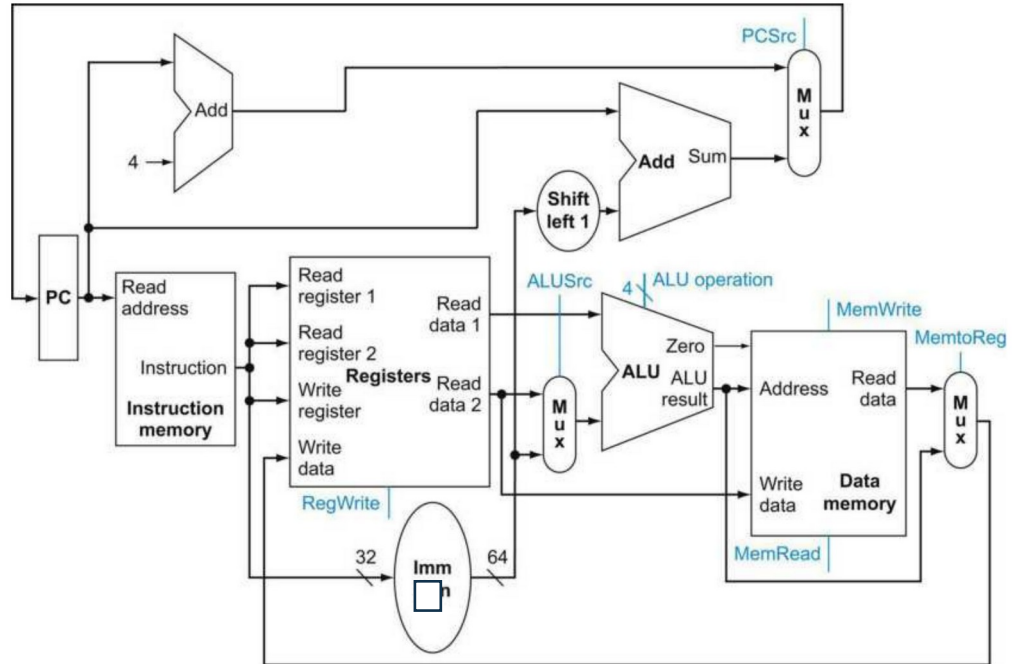
1. Fetch instruction from PC
2. Register file access
3. ALU execution
4. Memory access
5. Next PC update



Basic RISC-V CPU Datapath

Next PC calculation:

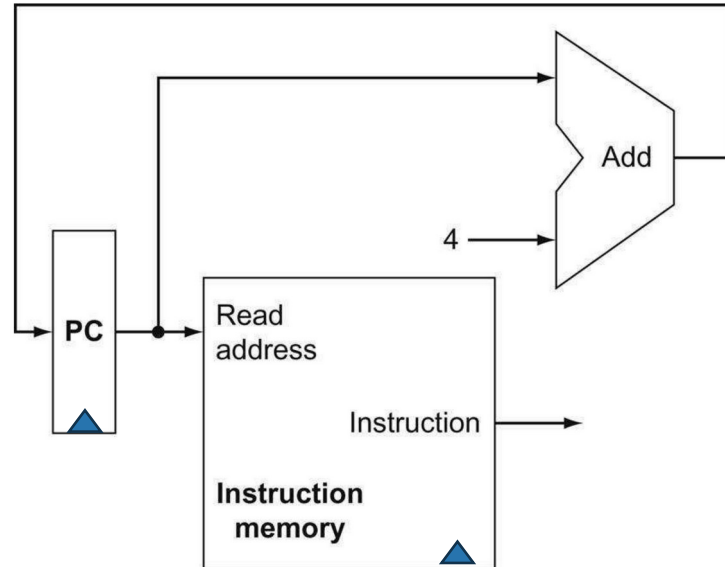
1. Program counter stored in PC
2. Can perform the addition in parallel
3. While reading the next instruction
4. Why adding 4 to PC?



Basic RISC-V CPU Datapath

Register File:

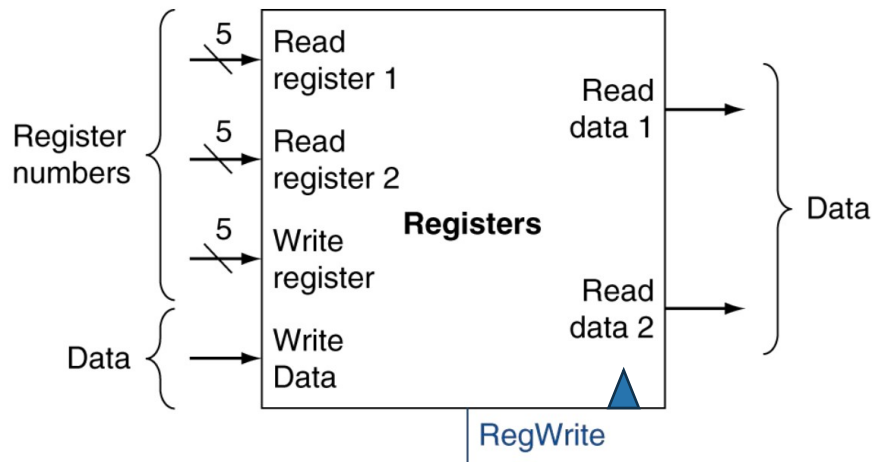- 32 total registers (5-bit addressing)
- 2x 5-bit source register addresses
- 1x 5-bit destination register address
- RegWrite: write enable
- **How to decode register address?**



Basic RISC-V CPU Datapath

Register File:


- How to decode register address?
 - No logic needed
 - **why?**

31	30	25	24	21	20	19	15	14	12	11	8	7	6	0			
funct7				rs2			rs1		funct3		rd			opcode		R-type	
imm[11:0]						rs1		funct3		rd			opcode		I-type		
imm[11:5]				rs2			rs1		funct3		imm[4:0]			opcode		S-type	
imm[12]		imm[10:5]			rs2			rs1		funct3		imm[4:1]		imm[11]		opcode	B-type
imm[31:12]										rd			opcode			U-type	
imm[20]		imm[10:1]			imm[11]		imm[19:12]			rd			opcode			J-type	

Basic RISC-V CPU Datapath

Branch operations:

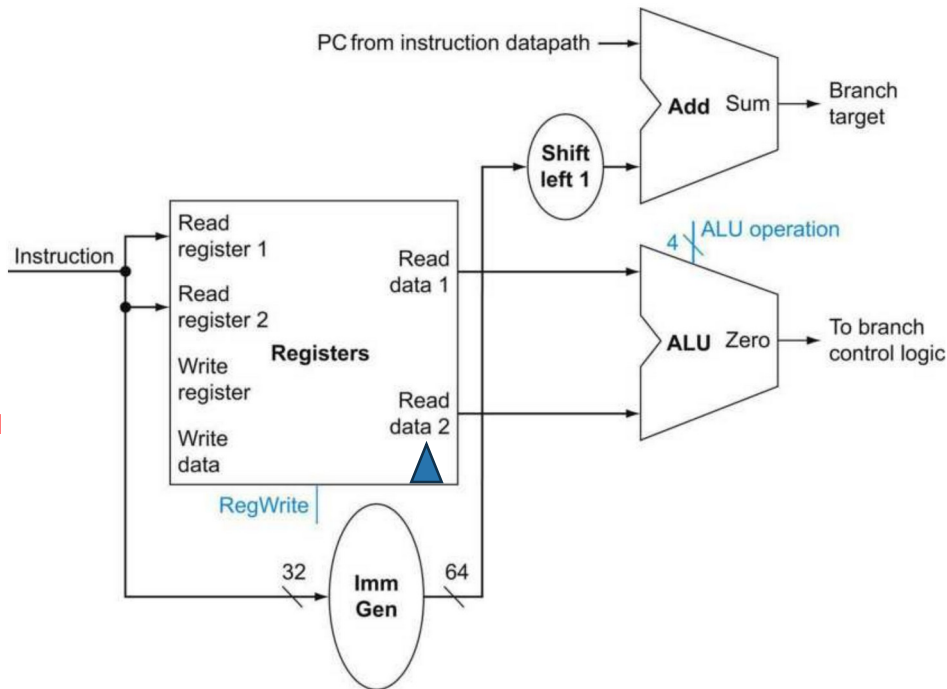
1. Register access
2. Immediate generation
3. Immediate shift
4. Branch target calculation
5. Branch condition evaluation
6. Why shift left 1?
7. Why not doing it inside Imm Gen?



Basic RISC-V CPU Datapath

Branch operations:

 
1. Register access
2. Immediate generation
3. Immediate shift
4. Branch target calculation
5. Branch condition evaluation
6. Parallelism?
7. Critical path?



Basic RISC-V CPU Datapath

Branch operations:

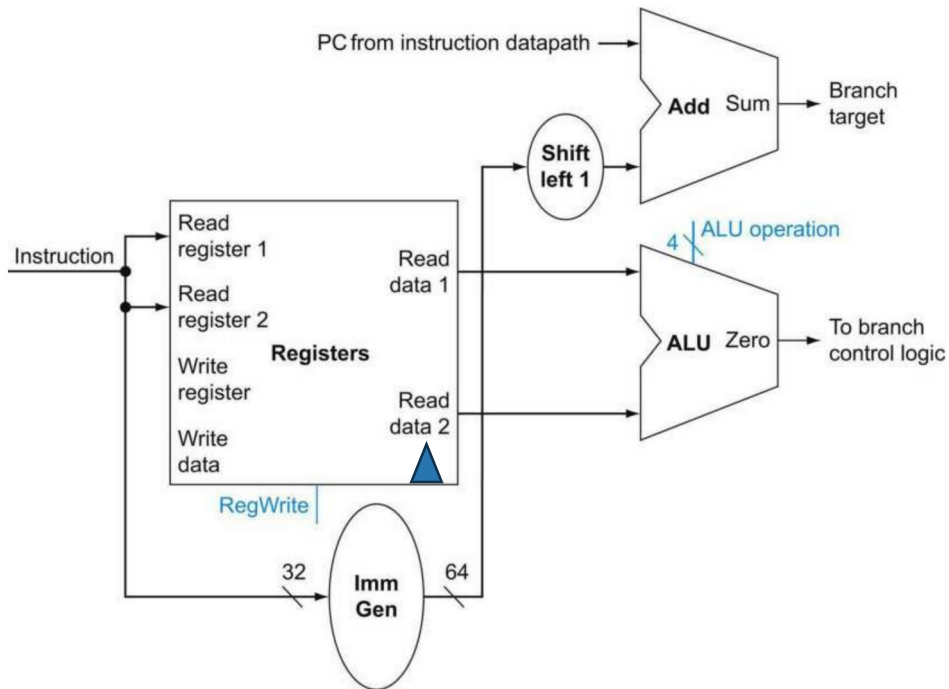
1. Register access
2. Immediate generation
3. Immediate shift
4. Branch target calculation
5. Branch condition evaluation
6. Parallelism
1->5, 2->3->4
7. Critical path
1->5



Basic RISC-V CPU Datapath

Memory Operations:

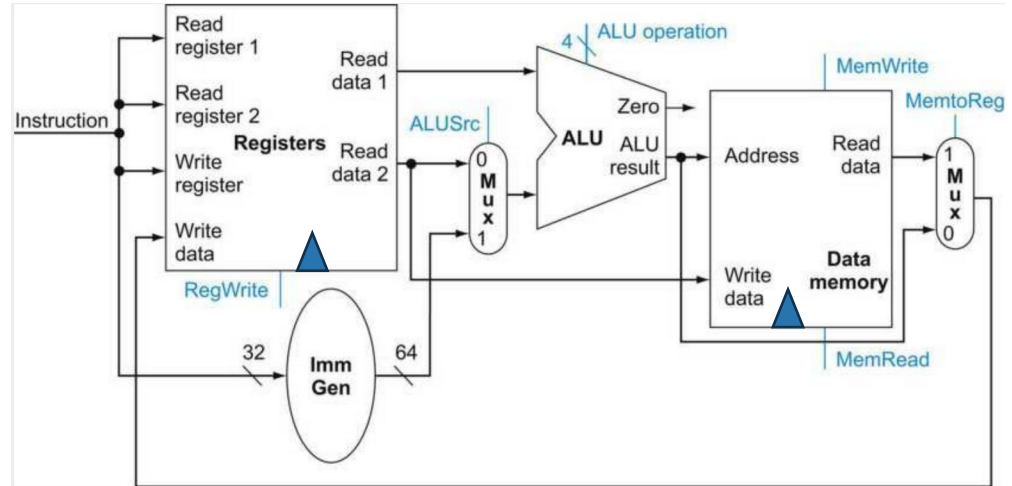
1. Address calculation
2. Memory access
3. ALUSrc select
 - 0: register
 - 1: immediate
4. Parallelism?
5. Critical path?



Basic RISC-V CPU Control Path

CPU control logic:

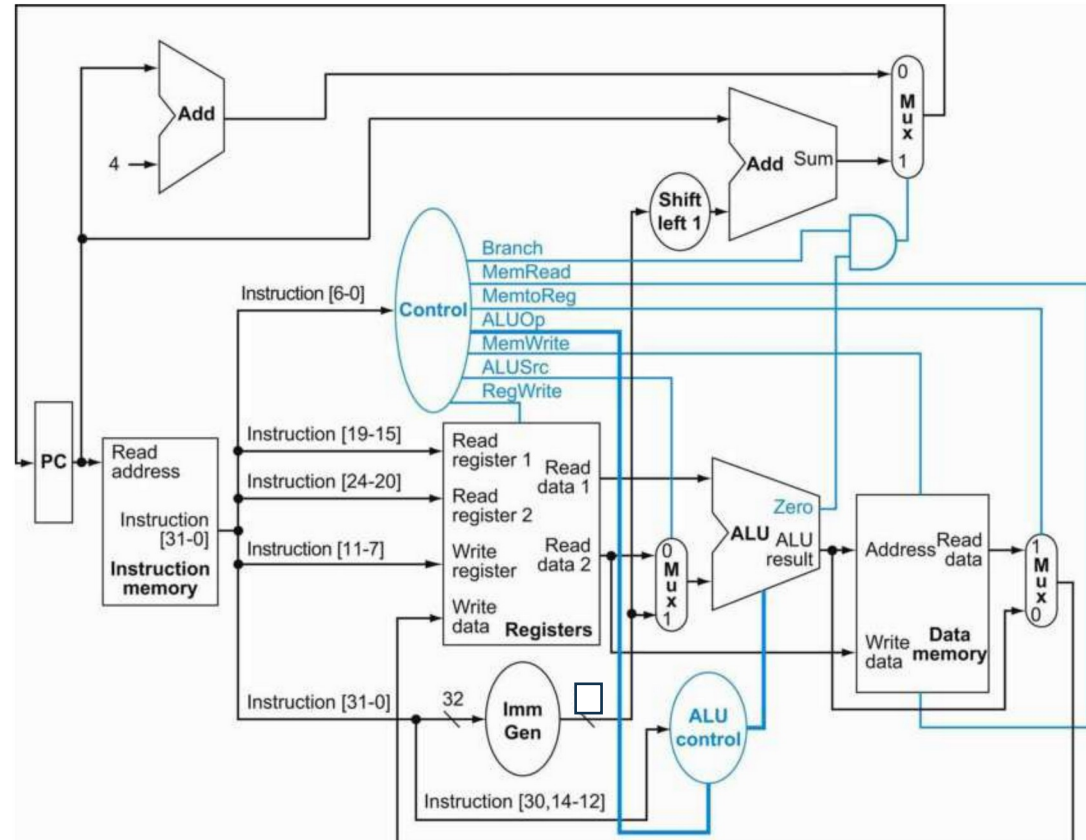- Main control
 - Register File
 - RegWrite
 - MemtoReg
 - ALU
 - ALUOp
 - ALUSrc
 - Data memory
 - MemRead
 - MemWrite
 - Branch
- ALU control
 - ALU operation



Basic RISC-V CPU Datapath

RISC-V ISA subset:

- R-type
- I-type
- LD/ST
- Branch

0000000	rs2	rs1	000	rd	0110011	ADD
0100000	rs2	rs1	000	rd	0110011	SUB
0000000	rs2	rs1	110	rd	0110011	OR
0000000	rs2	rs1	111	rd	0110011	AND


imm[11:0]	rs1	000	rd	0010011	ADDI
imm[11:0]	rs1	110	rd	0010011	ORI
imm[11:0]	rs1	111	rd	0010011	ANDI

imm[11:0]	rs1	010	rd	0000011	LW
imm[11:5]	rs2	rs1	010	imm[4:0]	SW

imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ
--------------	-----	-----	-----	-------------	---------	-----


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
R-Type	0110011						

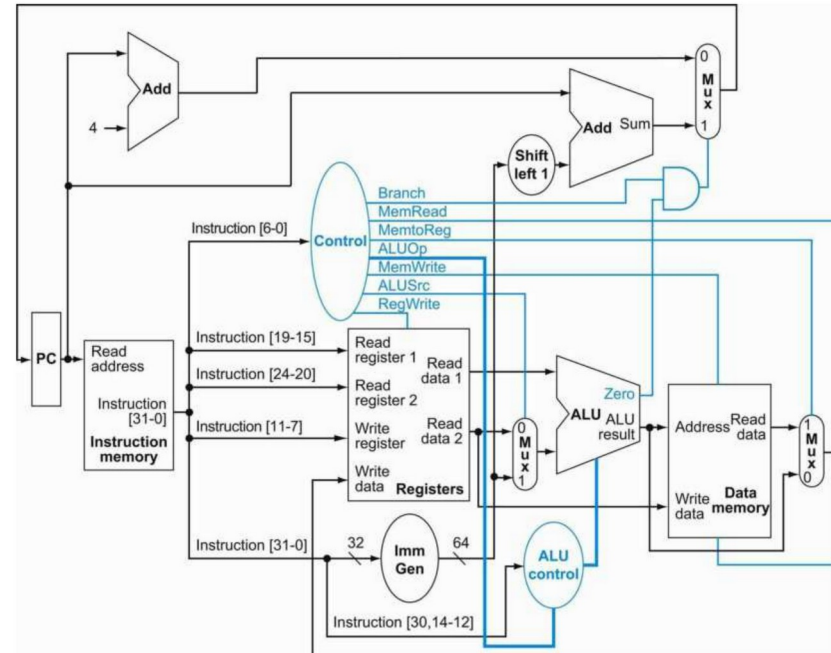


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
R-Type	0110011	1	0	0	0	0	0

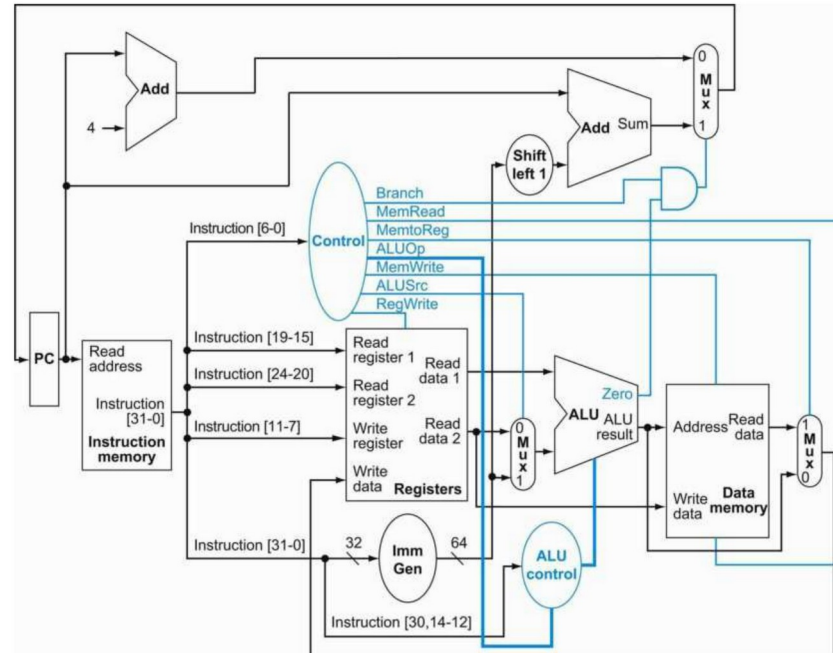


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
I-Type	0010011						

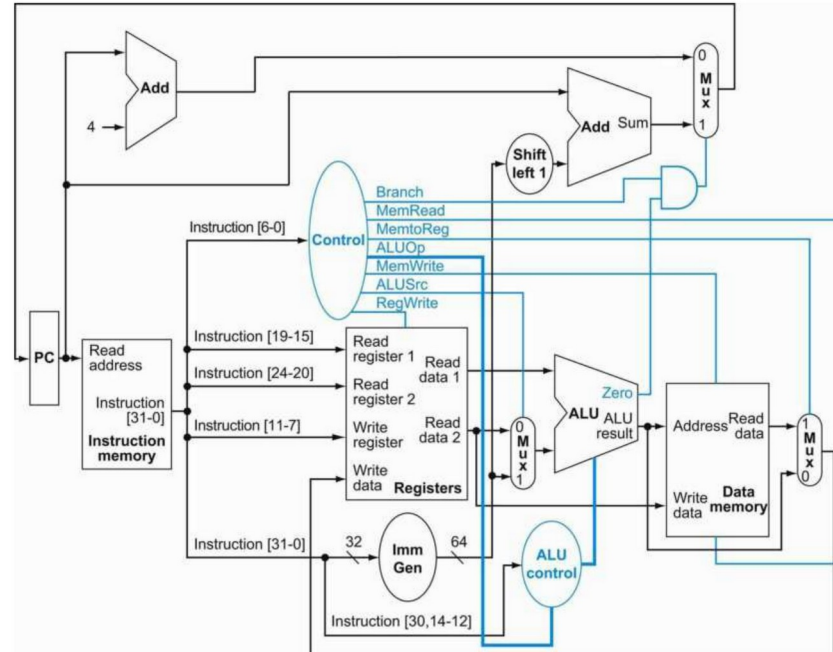


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
I-Type	0010011	1	1	0	0	0	0

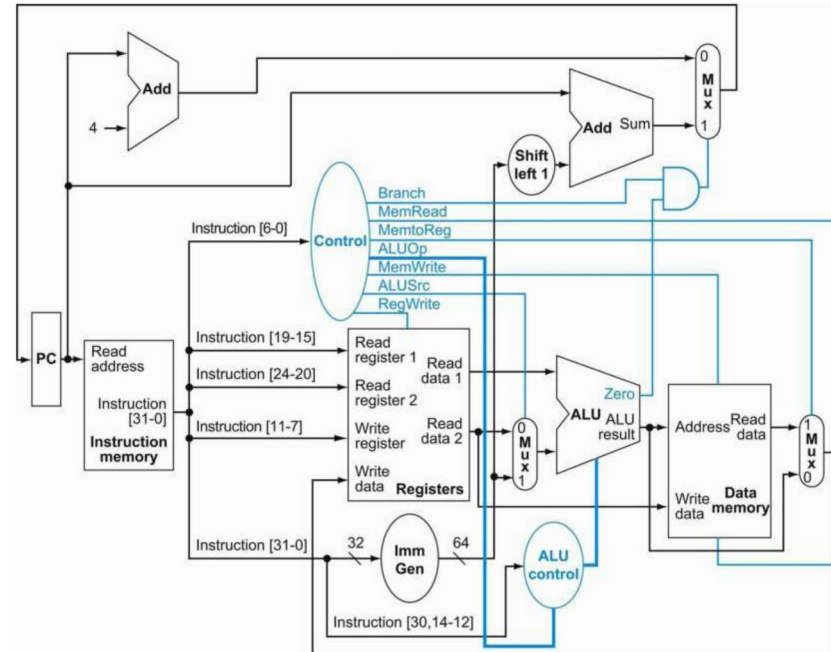


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
LW	0000011						

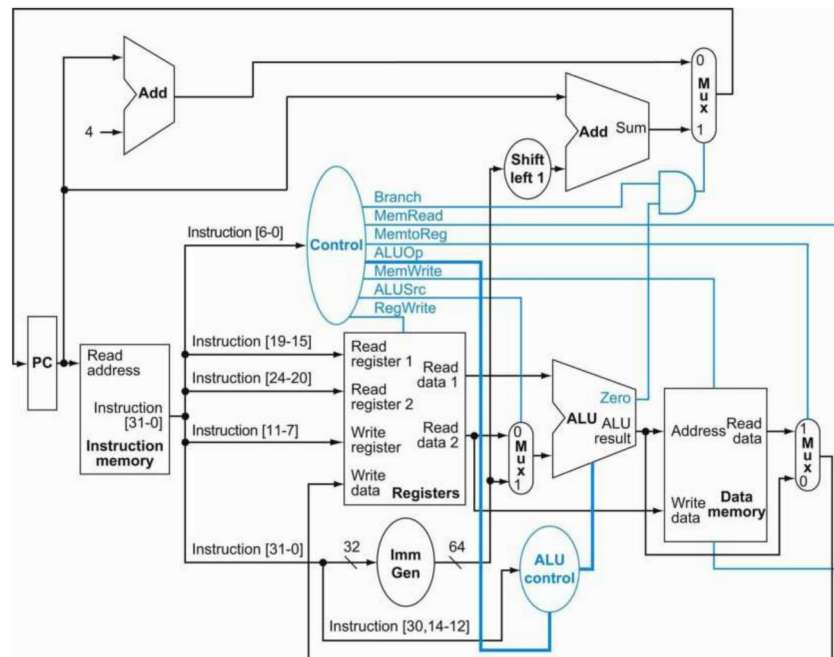


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
LW	0000011	1	1	0	1	0	1

 


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
SW	0100011						

 


Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
SW	0100011	0	1	0	0	1	0

 

Basic RISC-V CPU Control Path

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
BEQ	1100011	0	0	1	0	0	0

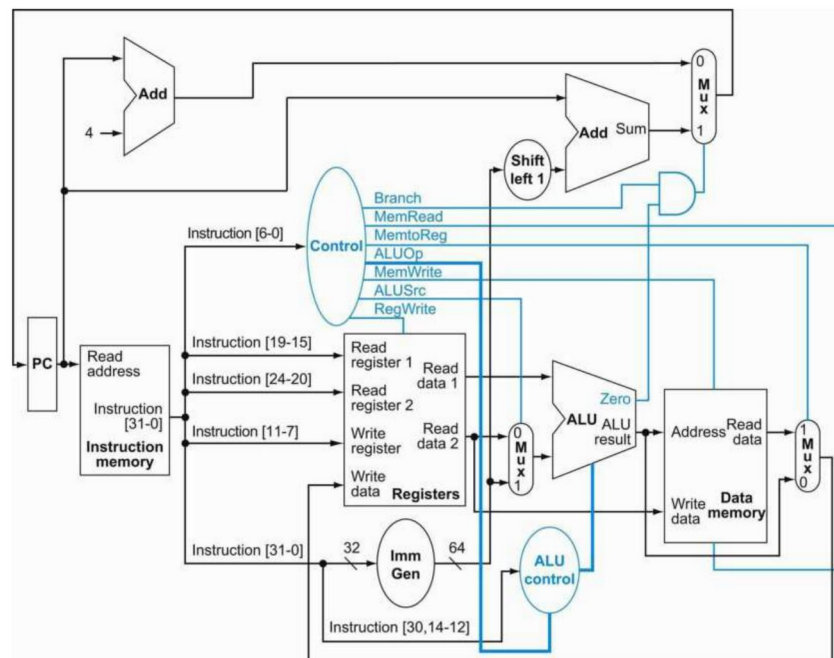

Basic RISC-V CPU Control Path

How to determine the type of instruction with minimal logic?

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
R-Type	0110011	1	0	0	0	0	0
I-Type	0010011	1	1	0	0	0	0
LW	0000011	1	1	0	1	0	1
SW	0100011	0	1	0	0	1	0
BEQ	1100011	0	0	1	0	0	0

Basic RISC-V CPU Control Path

- R-Type := intrs[4] & instrs[5]
- I-Type := ?
- LW := ?
- SW := ?
- BEQ := ?

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
R-Type	0110011	1	0	0	0	0	0
I-Type	0010011	1	1	0	0	0	0
LW	0000011	1	1	0	1	0	1
SW	0100011	0	1	0	0	1	0
BEQ	1100011	0	0	1	0	0	0

Basic RISC-V CPU Control Path

- R-Type := intrs[4] & instrs[5]
- I-Type := intr[4] & ~instr[5]
- LW := ~instr[4] & ~instr[5]
- SW := ?
- BEQ := ?

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg
R-Type	0110011	1	0	0	0	0	0
I-Type	0010011	1	1	0	0	0	0
LW	0000011	1	1	0	1	0	1
SW	0100011	0	1	0	0	1	0
BEQ	1100011	0	0	1	0	0	0

Basic RISC-V CPU Control Path

ALUOp =?

Only 4 operations:

- AND (00)
- OR (01)
- ADD (10)
- SUB (11)

BEQ := (rs1 - rs2)

Instruction	Opcode	Func3	Func7	ALU Fn	ALU Op
ADD	0110011	000	0000000	ADD	10
SUB	0110011	000	0100000	SUB	11
OR	0110011	110	0000000	OR	01
AND	0110011	111	0000000	AND	00
ADDI	0010011	000	xxxxxxx	ADD	10
ORI	0010011	110	xxxxxxx	OR	01
ANDI	0010011	111	xxxxxxx	AND	00
LW	0000011	010	xxxxxxx	ADD	10
SW	0100011	010	xxxxxxx	ADD	10
BEQ	1100011	000	xxxxxxx	SUB	11

Attendance

- Please Fill the form with today's keyword to register your attendance.




Single-Cycle Processor

Single-cycle Processor:

- Cycle I
 - Instruction memory read
 - Register file access
 - Control Units produce output
 - ALU produces output
 - Data memory read
 - Next PC calculation

Note: Assume Instruction and data memory read is asynchronous (same cycle), however memory updates are only visible in next cycle.

Advantages?

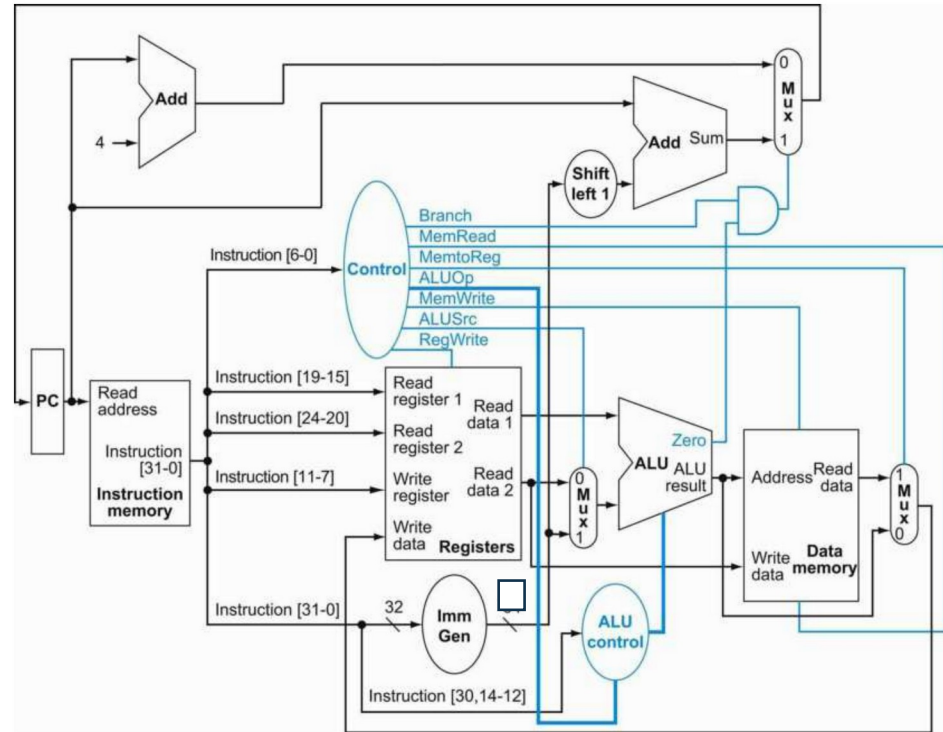


Single-Cycle Processor

Single-cycle Processor Advantages:

- Simple to implement
- Efficient design (resource usage)


Limitations?

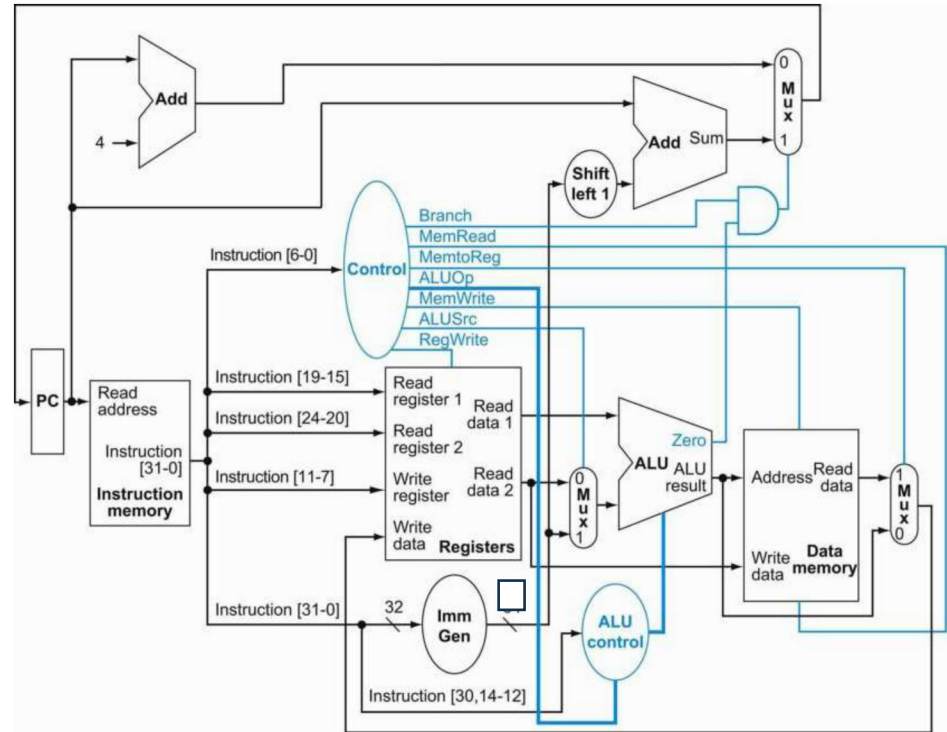

Single-Cycle Processor

Single-cycle Processor Limitations:

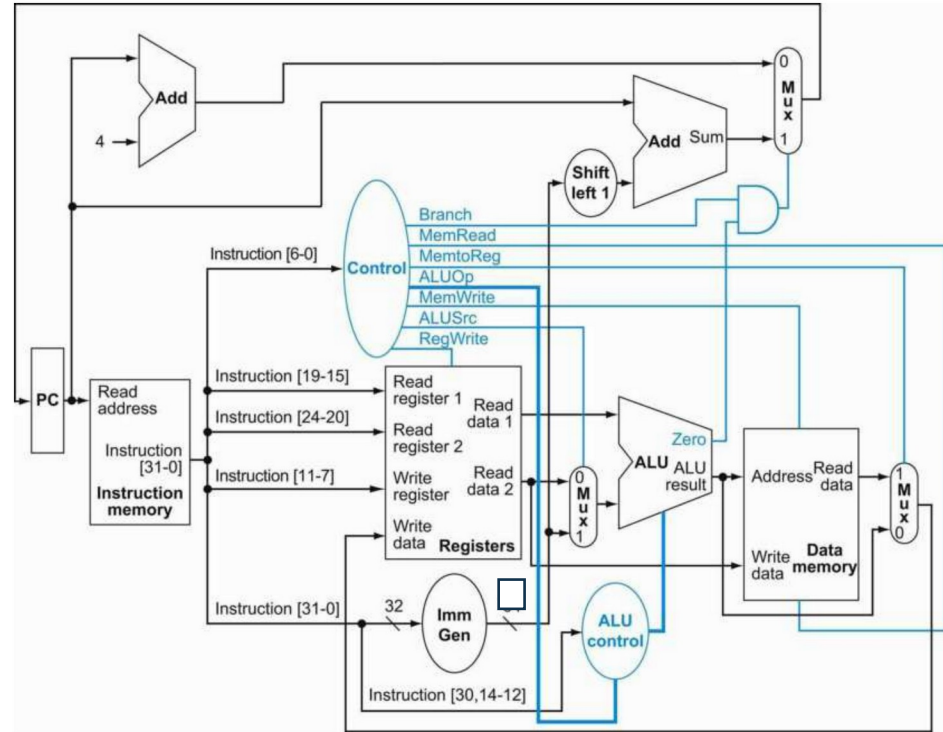- Weak performance
 - Long latency
- Critical path?




Single-Cycle Processor

Single-cycle Processor Latency:

- Long propagation delay
 - Signal propagation from source to destination
 - **Source**: input or register
 - **Destination**: output or register
- Imbalanced datapath
- Which path is the longest?

Why it affects latency?

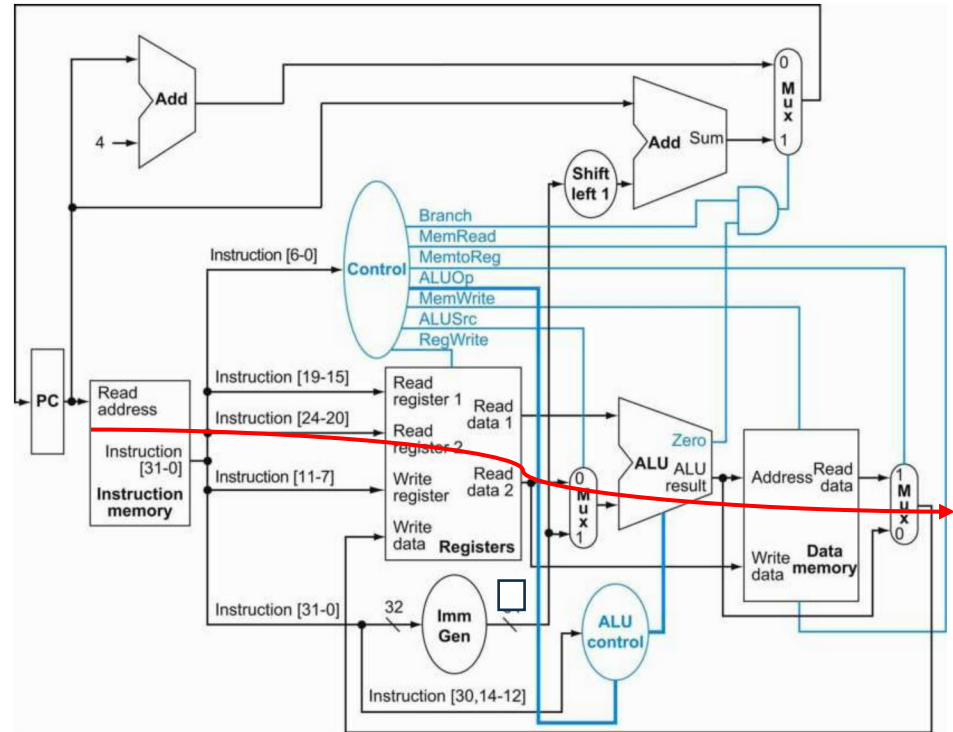


Single-Cycle Processor

Single-cycle Processor Latency:

- How this affects CPU latency?
- Longest delay determines the clock speed
- CPU clock affects performance

$$\text{CPU Time} = \text{InstCount} * \text{CPI} * \text{CycleTime}$$


How to reduce propagation delay?

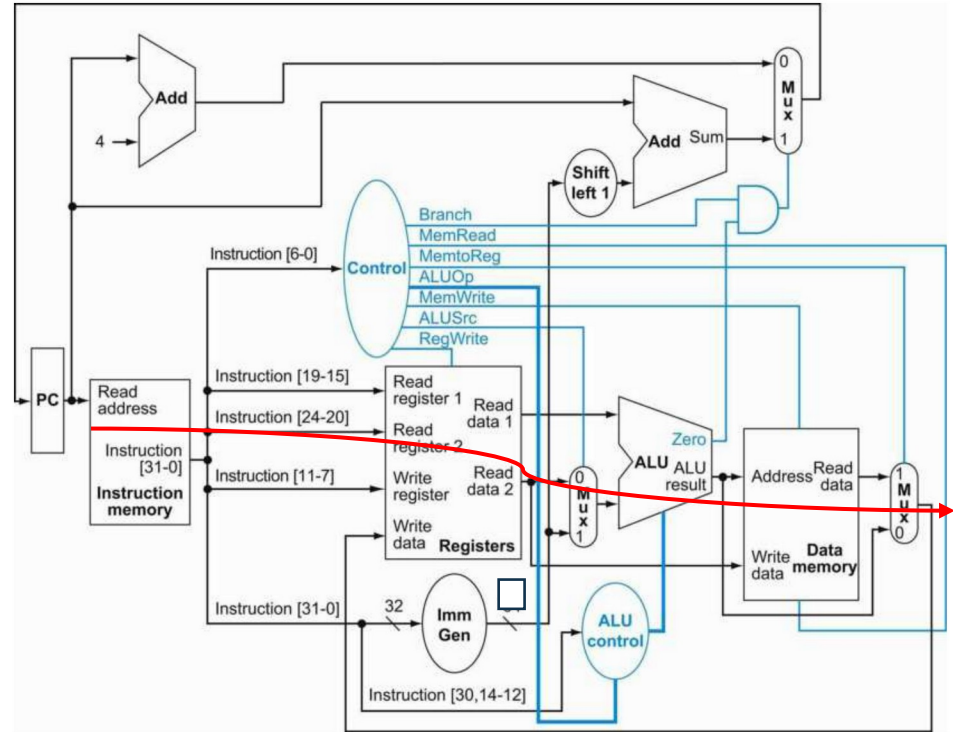

Single-Cycle Processor

Reducing Propagation Delay


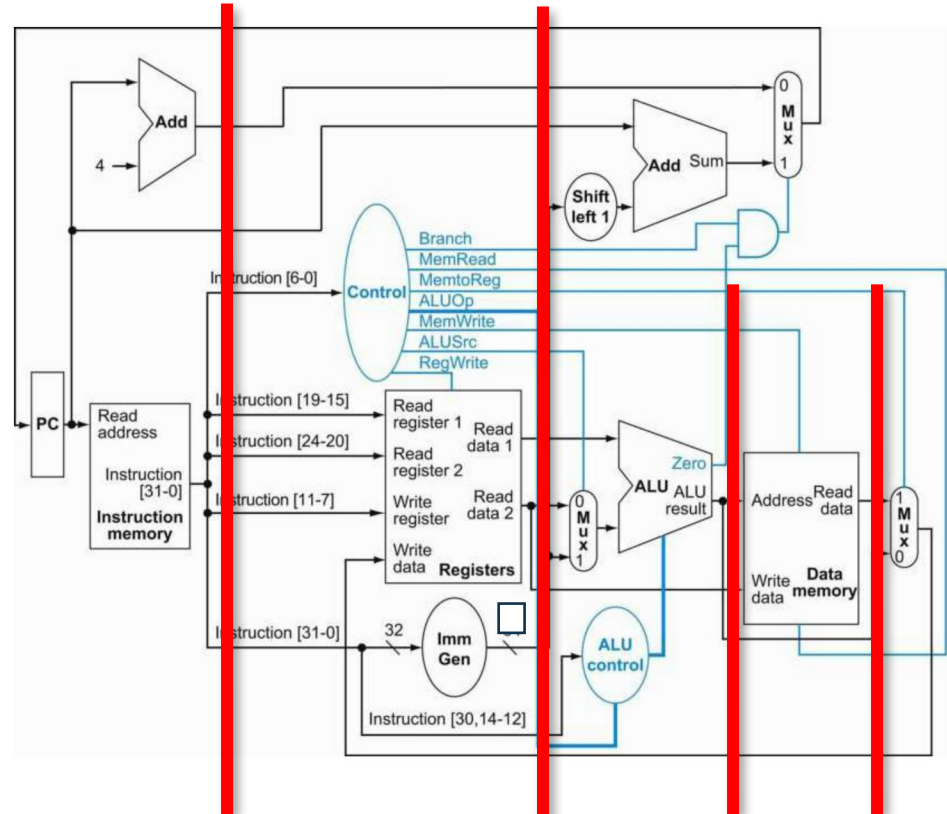
- Split the datapath into smaller chunks
- Insert registers in between
- Update control logic
 - Control registers inputs/outputs



Multi-Cycle Processor

Change to multi-cycle architecture

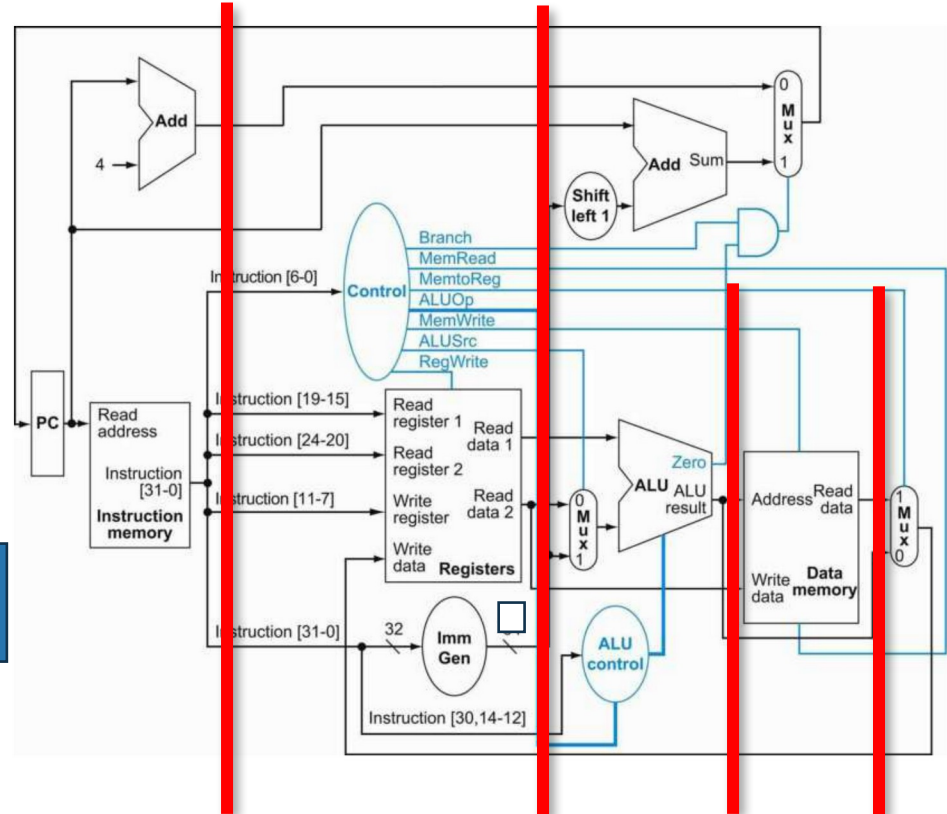 - 5 stages
 - IF: Instruction Fetch
 - ID: Register access
 - EX: ALU operation
 - MEM: Memory access
 - WB: Write back




Multi-Cycle Processor

Improved Propagation Delay

- Longest propagation delay?
 - $\max(\text{IF}, \text{ID}, \text{EX}, \text{MEM}, \text{WB})$
 - Should be smaller

How is the overall performance impacted?

 


Multi-Cycle Processor

Multi-cycle Processor Performance

- **Pros:** Cycle Time is reduced
- **Cons:** CPI is increased: a single instruction takes multiple cycles to complete

 
$$\text{CPU Time} = \text{InstCount} * \text{CPI} * \text{CycleTime}$$



Pipelined Processor

Observations?

 - **H/W resources are under utilized**
- When an instruction is stage WB
- IF, ID, E, and MEM stages are idle (do nothing)




Pipelined Processor

Solution

- Fetch a new instruction each cycle

 
e.g: Executing instructions sequence: I0, I1, I2, I3, I4



Pipelined Processor


How it work?

 - The PC should be incremented each cycle
- Online instructions are kept in pipeline registers




Pipelined Processor

Resource utilization

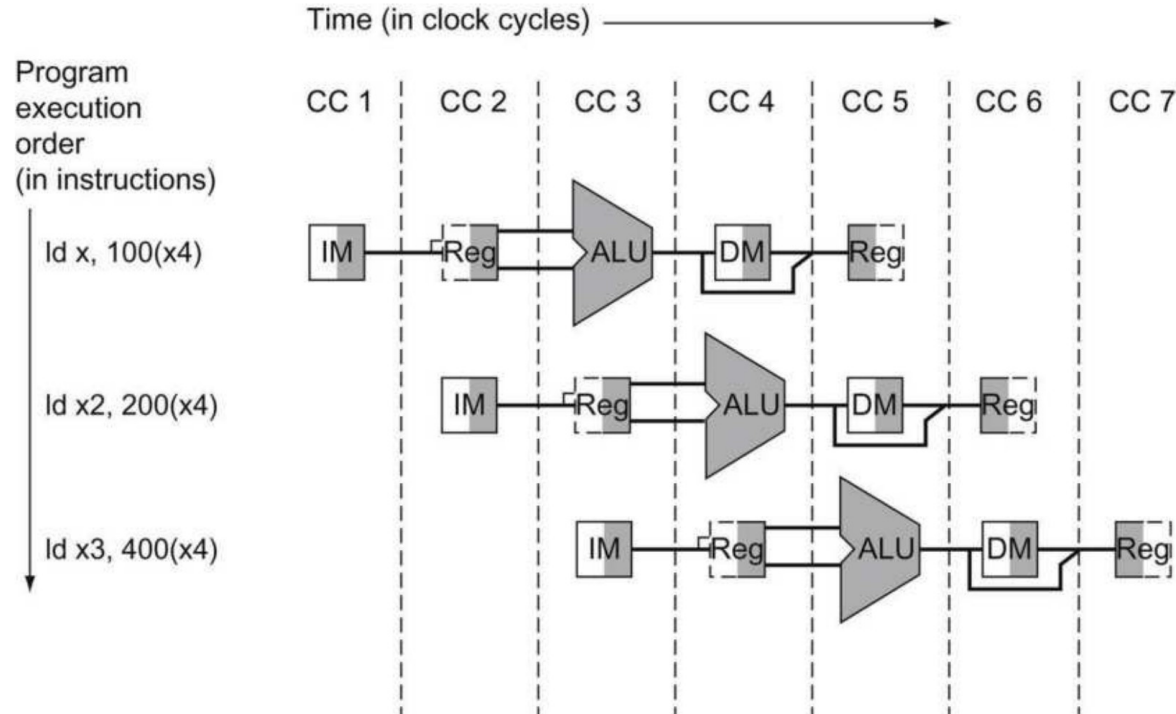

Pipelined Processor

Multi-cycle vs Pipelined performance

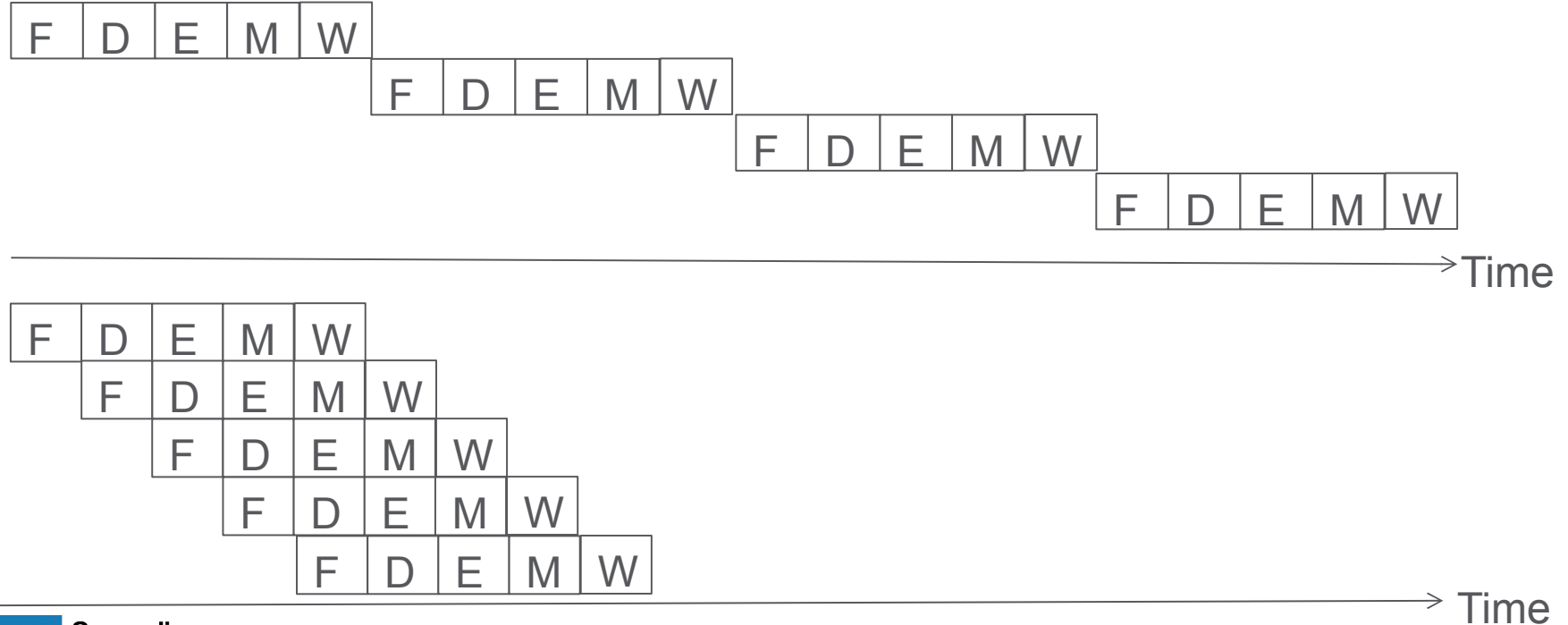

Pipelined Processor

Multi-cycle vs Pipelined performance


- The CPI is reduced
- Ideal pipelined CPI is 1
 - One instruction complete each cycle

$$\text{CPU Time} = \text{InstCount} * \text{CPI} * \text{CycleTime}$$

Exercise: Single-Cycle vs Pipeline

- Calculate cycle time (CT)


Unit	Latency (ps)
Instruction Fetch	400
Register Access	300
ALU	200
Memory Access	400

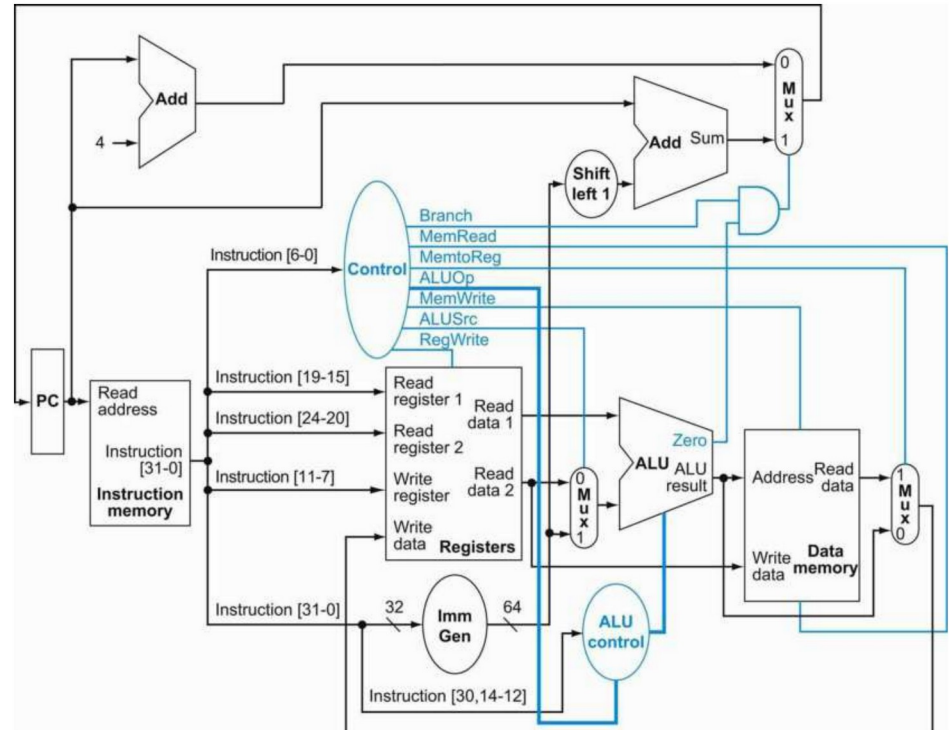

Exercise: Single-Cycle vs Pipeline

- Single-Cycle Datapath

Instr	Data Path
R/I-type	IF+RR+ALU+RW
LW	IF+RR+ALU+MR+RW
SW	IF+RR+ALU+MW
BEQ	IF+RR+ALU

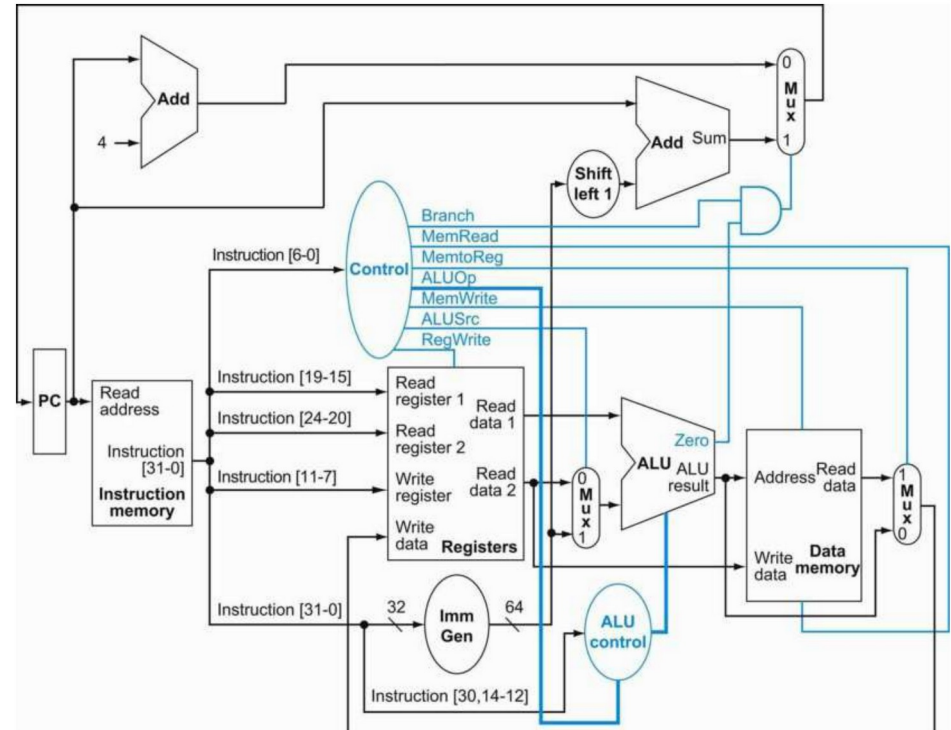

Exercise: Single-Cycle vs Pipeline

- Single-Cycle Datapath

Instr	Data Path	Cycle Time	Total Time
R/I-type	IF+RR+ALU+RW	400+300+200+300	1200 ps
LW	IF+RR+ALU+MR+RW	400+300+200+400+300	1600 ps
SW	IF+RR+ALU+MW	400+300+200+400	1300 ps
BEQ	IF+RR+ALU	400+300+200	900 ps

Exercise: Single-Cycle vs Pipeline

- Pipeline Datapath


Instr	Data Path	Cycle Time	Total Time
R/I-type	IF RR ALU RW	Max(400,300,200,300)	400 ps
LW	IF RR ALU MR RW	Max(400,300,200,400,300)	400 ps
SW	IF RR ALU MW	Max(400,300,200,400)	400 ps
BEQ	IF RR ALU	Max(400,300,200)	400 ps



5-Stage Pipeline RISC-V Processor


Pipelined control logic

- Propagate the flags along the pipeline

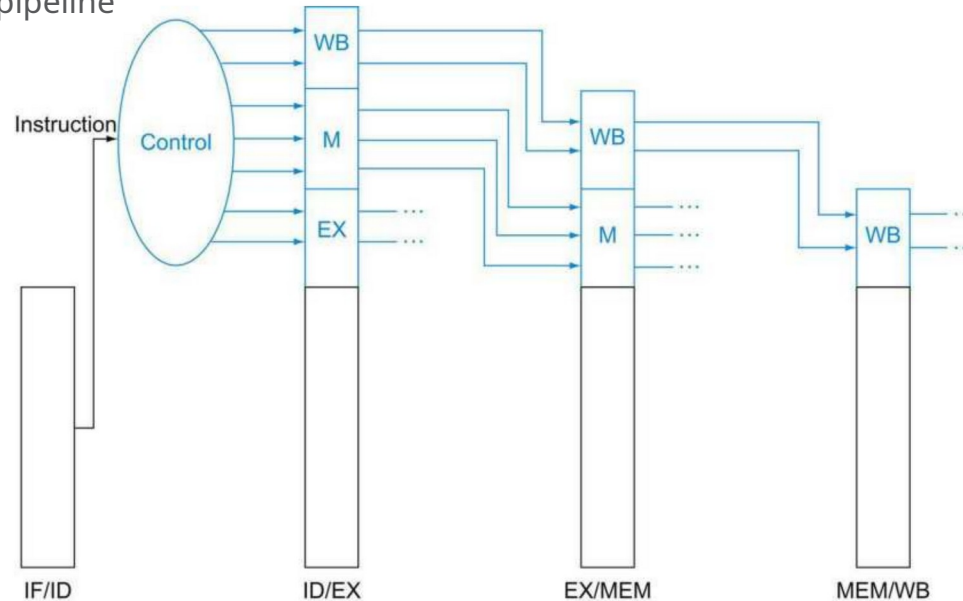

Basic RISC-V CPU Data & Control Path

Data path
Control Path

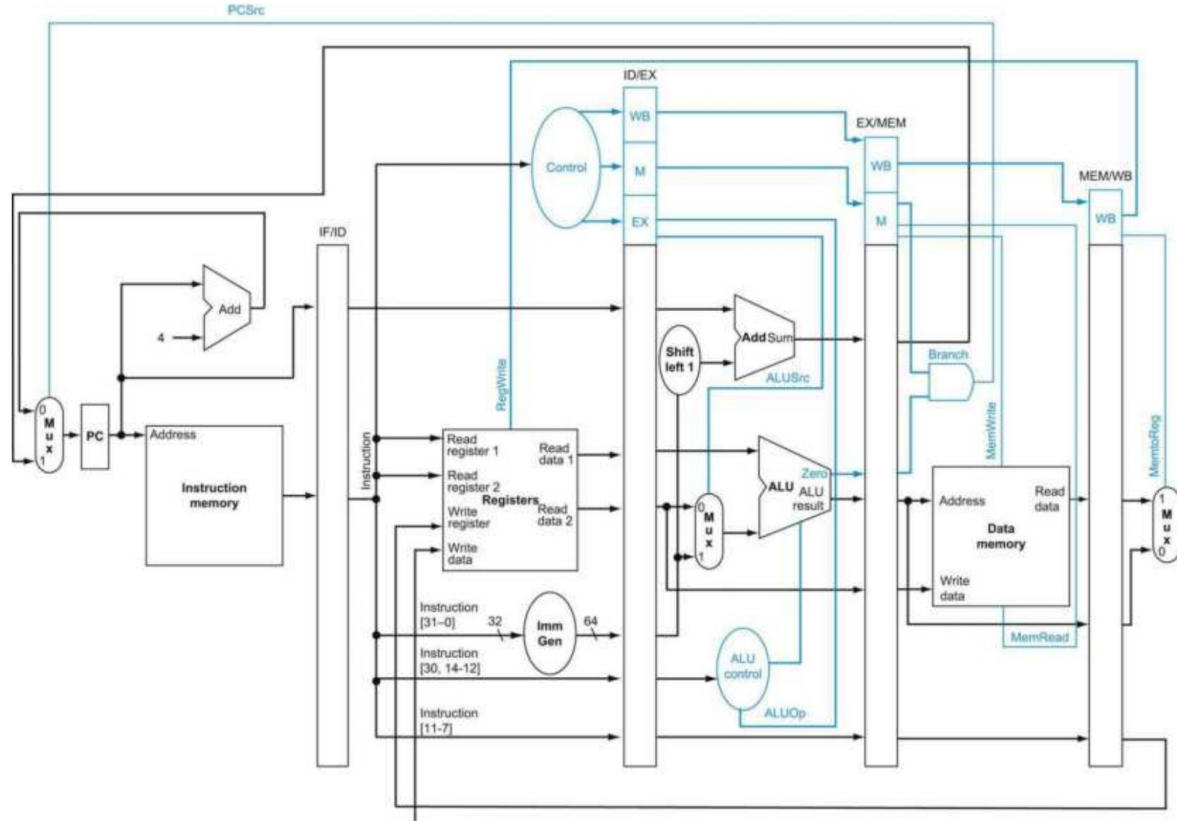

Q&A
